

30 Days of RTL Coding

-By T Tushar Shenoy

Day 18

Problem Statement: Implementing Comparator in Behavioural style of Implementation.

Theory:

1-Bit Magnitude Comparator

A comparator used to compare two bits is called a single-bit comparator. It consists of two inputs each for two single-bit numbers and three outputs to generate less than, equal to, and greater than between two binary numbers.

Truth Table

A	B	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

Verilog Code:

//Verilog Code for 1 Bit Comparator

```
module comparator1bit(A,B,AeB,AgB,AlB);
```

```
input A,B;
```

```
output reg AeB,AgB,AlB;
```

```
always@(A,B)
```

```
begin
```

```
AeB=1'b0;AgB=1'b0;AlB=1'b0;
```

```
case({A,B})
```

```
2'b00:AeB<=1'b1;
```

```
2'b01:AlB=1'b1;
```

```
2'b10:AgB=1'b1;
```

```
2'b11:AeB<=1'b1;
```

```
endcase
```

```
end
```

```
endmodule
```

Testbench Code:

//Testbench code for 1 Bit Comparator

```
module comparator1bit_tb();
```

```
    reg A,B;
```

```
    wire AeB,AgB,AlB;
```

```
    comparator1bit dut(.A(A),.B(B),.AeB(AeB),.AgB(AgB),.AlB(AlB));
```

```
    initial begin
```

```
        A=1'b0;B=1'b0;
```

```
        #5 A=1'b0;B=1'b1;
```


```
        #5 A=1'b1;B=1'b0;
```

```
        #5 A=1'b1;B=1'b1;
```

```
        #5 $finish;
```

```
    end
```

```
endmodule
```

 

2-Bit Magnitude Comparator

A comparator used to compare two binary numbers each of two bits is called a 2-bit Magnitude comparator. It consists of four inputs and three outputs to generate less than, equal to, and greater than between two binary numbers.

Truth Table

Inputs				Outputs		
A		B				
a1	a0	b1	b0	A = B	A > B	A < B
0	0	0	0	1	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	1	0	0

Verilog Code:

//Verilog Code for 2 Bit Comparator

```
module comparator2bit(A,B,AeB,AgB,AlB);
```

```
input [1:0]A,B;
```

```
output reg AeB,AgB,AlB;
```

```
always@(A,B)
```

```
begin
```

```
AeB=1'b0;AgB=1'b0;AlB=1'b0;
```

```
if(A==B)
```

```
    AeB=1'b1;
```

```
else if(A<B)
```

```
    AlB=1'b1;
```

```
else
```

```
    AgB=1'b1;
```

```
end
```

```
endmodule
```

Testbench Code:

//Testbench code for 2 Bit Comparator

```
module comparator2bit_tb();
```

```
    reg [1:0]A,B;
```

```
    wire AeB,AgB,AlB;
```

```
    comparator2bit dut(.A(A),.B(B),.AeB(AeB),.AgB(AgB),.AlB(AlB));
```

```
    initial begin
```

```
        A=2'b00;B=2'b11;
```

```
        #5 A=2'b01;B=2'b10;
```

```
        #5 A=2'b10;B=2'b01;
```

```
        #5 A=2'b11;B=2'b00;
```



```
        #5 A=2'b00;B=2'b00;
```

```
        //Add More Test Cases Here
```

```
        #5 $finish;
```

```
    end
```

```
endmodule
```

 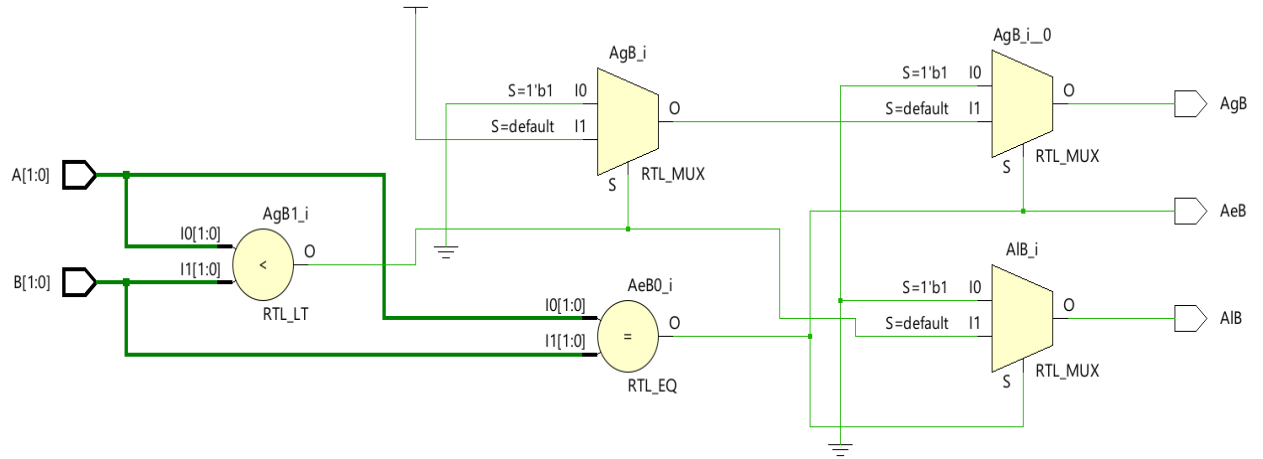

4-Bit Magnitude Comparator

A comparator used to compare two binary numbers each of four bits is called a 4-bit magnitude comparator. It consists of eight inputs each for two four-bit numbers and three outputs to generate less than, equal to, and greater than between two binary numbers.

Verilog Code:

```
//Verilog Code for 4 Bit Comparator
module comparator4bit(A,B,AeB,AgB,AlB);

input [3:0]A,B;
output reg AeB,AgB,AlB;

always@(A,B)
begin
AeB=1'b0;AgB=1'b0;AlB=1'b0;
if(A==B)
    AeB=1'b1;
else if(A<B)
    AlB=1'b1;
else
    AgB=1'b1;
end

endmodule
```

Testbench Code:

```
//Testbench code for 4 Bit Comparator
```

```
module comparator4bit_tb();
```

```
reg [3:0]A,B;
```

```
wire AeB,AgB,AlB;
```

```
comparator4bit dut(.A(A),.B(B),.AeB(AeB),.AgB(AgB),.AlB(AlB));
```

```
initial begin
```

```
    A=4'b0000;B=4'b1111;
```

```
#5 A=4'b0001;B=4'b1110;
```

```
#5 A=4'b0010;B=4'b1101;
```

```
#5 A=4'b0011;B=4'b1100;
```

```
#5 A=4'b0100;B=4'b1011;
```

```
#5 A=4'b0101;B=4'b1010;
```

```
#5 A=4'b0110;B=4'b1001;
```

```
#5 A=4'b0111;B=4'b1000;
```

```
#5 A=4'b1000;B=4'b0111;
```

```
#5 A=4'b1001;B=4'b0110;
```

```
#5 A=4'b1010;B=4'b0101;
```

```
#5 A=4'b1011;B=4'b0100;
```

```
#5 A=4'b1100;B=4'b0011;
```

```
#5 A=4'b1101;B=4'b0010;
```

```
#5 A=4'b1110;B=4'b0001;
```


```
#5 A=4'b1111;B=4'b0000;
```

```
#5 A=4'b1111;B=4'b1111;
```


end

endmodule

Schematic:

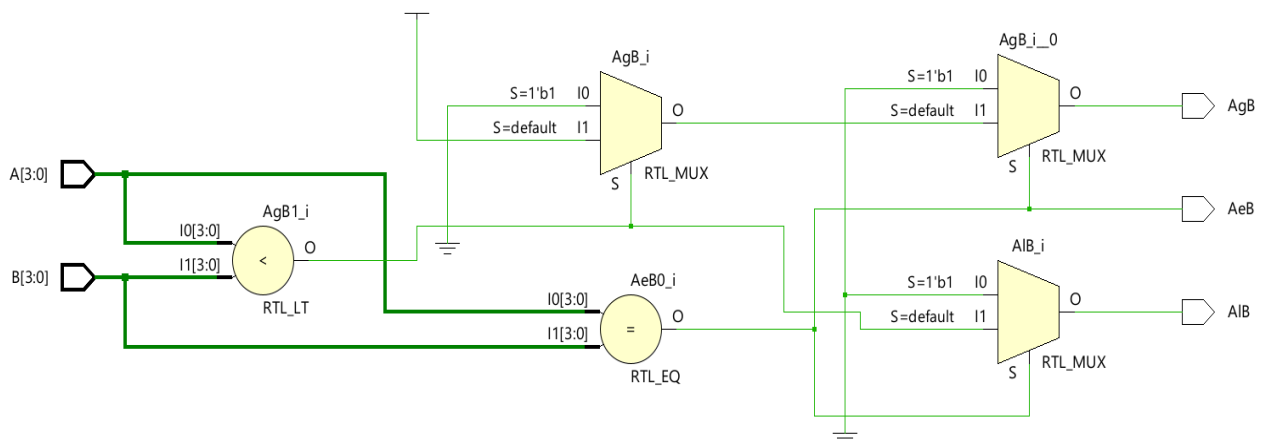

Simulation Output:

 

GitHub Repository URL: <https://github.com/tusharshenoy/RTL-Day-18-Comparator-Behavioral-I>