

30 Days of RTL Coding

-By T Tushar Shenoy

Day 14

Problem Statement: Implementing a 2 to 4 Decoder, 3 to 8 Decoder and 4 to 16 Decoder using Gate/Structural Implementation.

Theory:

The combinational circuit that change the binary information into 2^N output lines is known as **Decoders**. The binary information is passed in the form of N input lines. The output lines define the 2^N -bit code for the binary information. In simple words, the **Decoder** performs the reverse operation of the **Encoder**. At a time, only one input line is activated for simplicity. The produced 2^N -bit output code is equivalent to the binary information.

 


FIG: Decoder Block Diagram

1. 2 to 4 line decoder:

In the 2 to 4 line decoder, there is a total of three inputs, i.e., A_0 , and A_1 and E and four outputs, i.e., Y_0 , Y_1 , Y_2 , and Y_3 . For each combination of inputs, when the enable 'E' is set to 1, one of these four outputs will be 1.

 


FIG: 2 to 4 Decoder Block Diagram

Truth Table:

Enable	INPUTS		OUTPUTS			
E	A ₁	A ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 


FIG: 2 to 4 Decoder Logic Diagram

Verilog Code:

//Verilog code for 2 to 4 Decoder

```
module Decoder2to4(A,E,Y);
```

```
    input [1:0]A;
```

```
    input E;
```

```
    output [3:0]Y;
```

```
    wire [1:0]w;
```

```
    not N0(w[0],A[0]);
```

```
    not N1(w[1],A[1]);
```

```
    and A3(Y[3],A[0],A[1],E);
```

```
    and A2(Y[2],A[1],w[0],E);
```

```
    and A1(Y[1],A[0],w[1],E);
```

```
    and A0(Y[0],w[0],w[1],E);
```

```
endmodule
```

Testbench Code:

// Testbench Code for 2 to 4 Decoder

```
module Decoder2to4_tb();
```

```
    reg [1:0]A;
```

```
    reg E;
```

```
    wire [3:0]Y;
```

```
    Decoder2to4 dut(.A(A),.E(E),.Y(Y));
```

```
    initial begin
```

```
        E=1'b0;
```

```
        A=2'bxx;
```

```
        #5 E=1'b1;
```

```
        A=2'b00;
```

```
        #5 A=2'b01;
```

```
        #5 A=2'b10;
```

```
        #5 A=2'b11;
```

```
        #5 $finish;
```

```
    end
```

```
endmodule
```

Schematic:


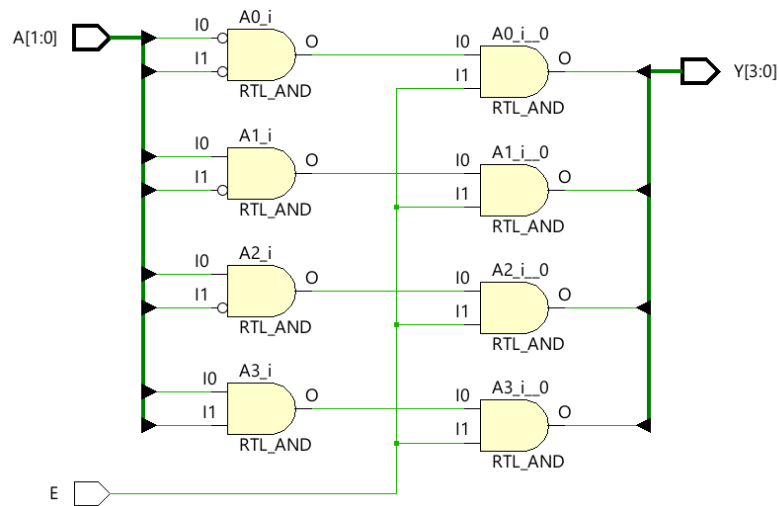


FIG: 2 to 4 Decoder Schematic

Simulation Output:

 

2. 3 to 8 line decoder:

The 3 to 8 line decoder is also known as binary to Octal Decoder. In a 3 to 8 line decoder, there is a total of eight outputs, i.e., Y_0 , Y_1 , Y_2 , Y_3 , Y_4 , Y_5 , Y_6 , and Y_7 and three outputs, i.e., A_0 , A_1 , and A_2 . This circuit has an enable input 'E'. Just like 2 to 4 line decoder, when enable 'E' is set to 1, one of these four outputs will be 1.

 


FIG: 3 to 8 Decoder Block Diagram

Truth Table:

Enable	INPUTS			Outputs							
E	A_2	A_1	A_0	Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

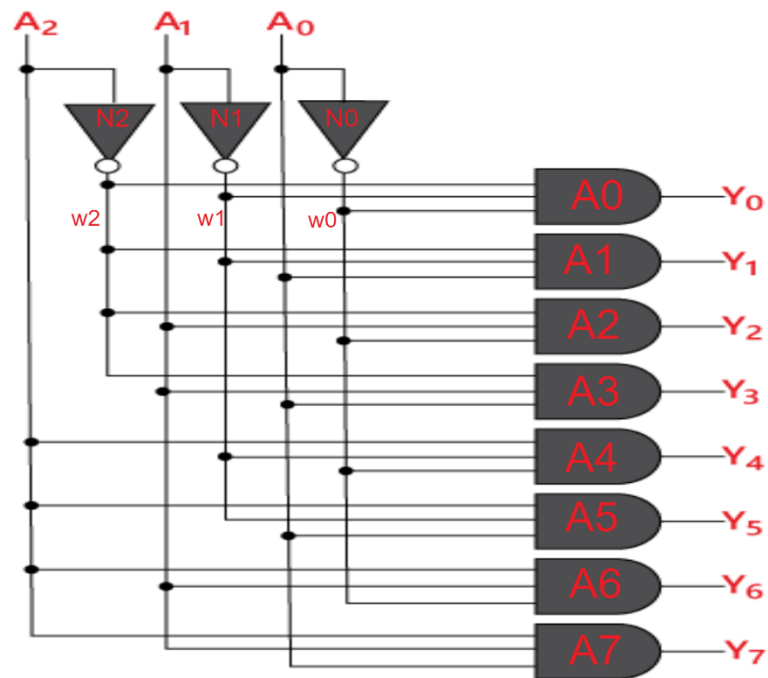


FIG: 3 to 8 Decoder Logic Diagram

Verilog Code:

// Verilog Code for 8x3 Encoder

```
module Encoder8x3(Y,A);
```

```
input [7:0]Y;
```

```
output [2:0]A;
```

```
or O2(A[2],Y[7],Y[6],Y[5],Y[4]);
```

```
or O1(A[1],Y[7],Y[6],Y[3],Y[2]);
```

```
or O0(A[0],Y[7],Y[5],Y[3],Y[1]);
```

```
endmodule
```

Testbench Code:

//Testbench for 8x3 Encoder

```
module Encoder8x3_tb();
```

```
    reg [7:0]Y;
```

```
    wire [2:0]A;
```

```
    Encoder8x3 dut(.Y(Y),.A(A));
```

```
    initial begin
```

```
        Y=8'b00000001;
```

```
        #5 Y=8'b00000010;
```

```
        #5 Y=8'b00000100;
```

```
        #5 Y=8'b00001000;
```

```
        #5 Y=8'b00010000;
```

```
        #5 Y=8'b00100000;
```

```
        #5 Y=8'b01000000;
```

```
        #5 Y=8'b10000000;
```

```
        #5 $finish;
```

```
    end
```

```
endmodule
```


Schematic:

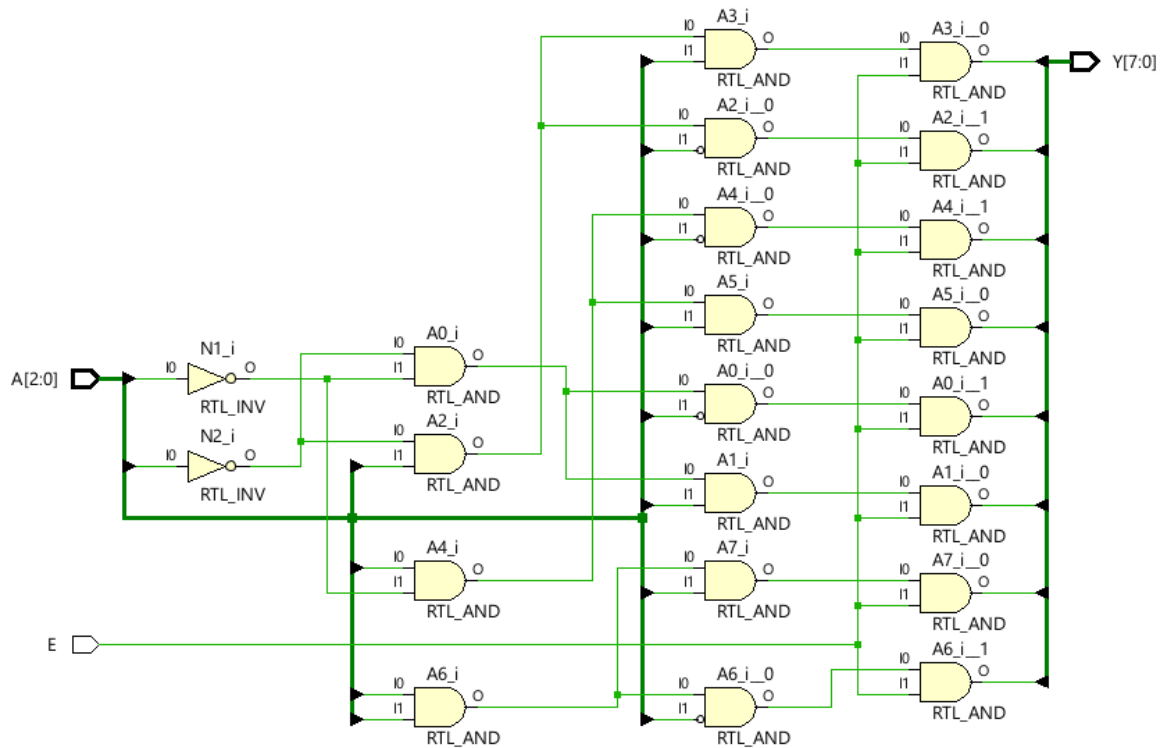


FIG: 3 to 8 Decoder Schematic

Simulation Output:

		0.000 ns									
Name	Value	0.000 ns	5.000 ns	10.000 ns	15.000 ns	20.000 ns	25.000 ns	30.000 ns	35.000 ns	40.000 ns	45.000 ns
> A[2:0]	XXX	xxx	000	001	010	011	100	101	110	111	
E	0										
> Y[7:0]	00000000	00000000	00000001	00000010	00000100	00001000	00010000	00100000	01000000	10000000	

3. **4 to 16 line decoder** In the 4 to 16 line decoder, there is a total of 16 outputs, i.e., $Y_0, Y_1, Y_2, \dots, Y_{16}$ and four inputs, i.e., A_0, A_1, A_2 , and A_3 . The 3 to 16 line decoder can be constructed using either 2 to 4 decoder or 3 to 8 decoder.

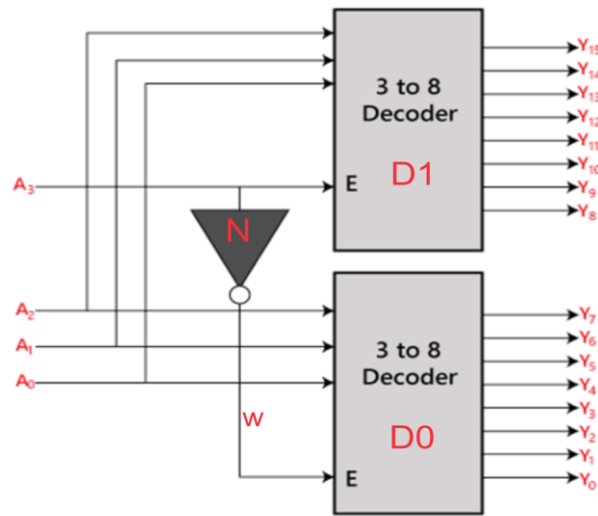


FIG: 4 to 16 line decoder Block Diagram

Truth Table

[illegible]

 


FIG: 4 to 16 line decoder Logic Diagram

Verilog Code:

```
// Verilog Code for 4 to 16 Decoder
// Structural Style using Decoder3to8 Structure
module Decoder4to16(A,Y);

input [3:0]A;

output [15:0]Y;

Decoder3to8 D1(.A(A[2:0]),.E(A[3]),.Y(Y[15:8]));
wire w;
not N(w,A[3]);
Decoder3to8 D0(.A(A[2:0]),.E(w),.Y(Y[7:0]));
endmodule
```

Testbench Code:

// Testbench Code for 4 to 16 Decoder

```
module Decoder4to16_tb();
```

```
    reg [3:0]A;
```

```
    wire [15:0]Y;
```

```
    integer i;
```

```
    Decoder4to16 dut(.A(A),.Y(Y));
```

```
    initial begin
```

```
        A=4'b1111;
```

```
        for(i=0;i<16;i=i+1)
```

```
        begin
```

```
            A=A+1;
```

```
            #5;
```

```
        end
```

```
    $finish;
```

```
end
```

```
endmodule
```

Schematic:

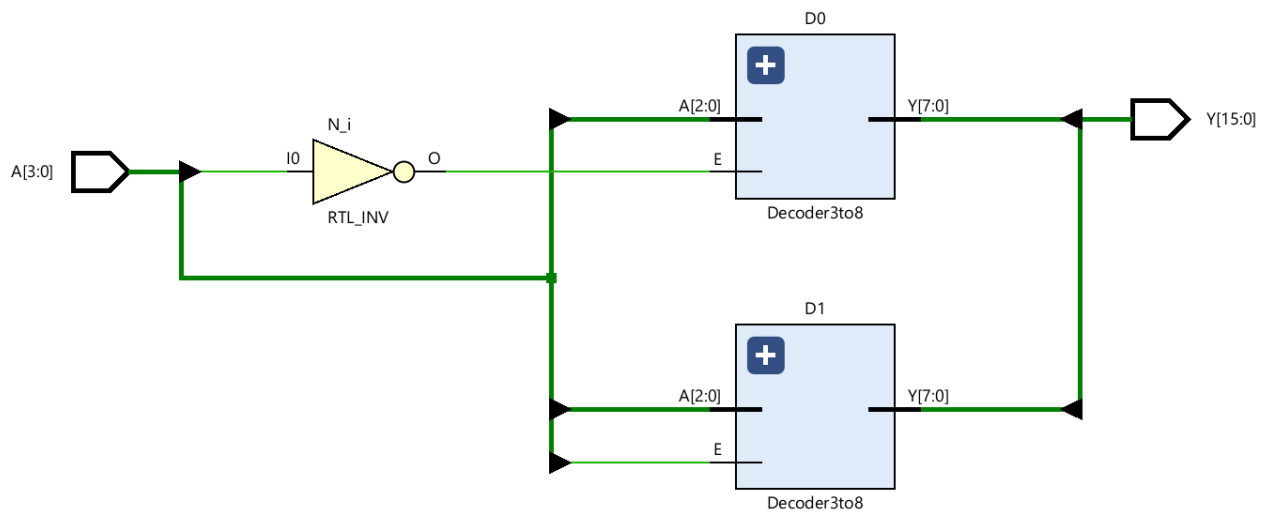


FIG: 4 to 16 Decoder Schematic


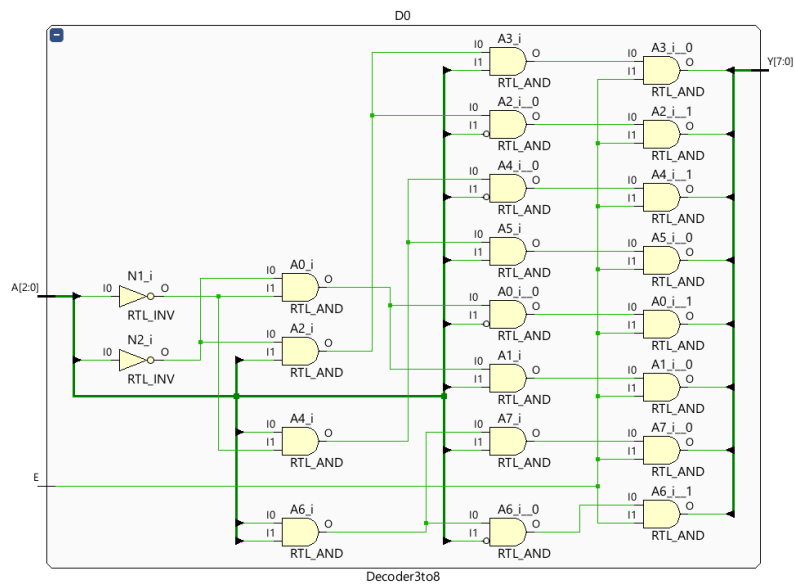
 


FIG: 3 to 8 Decoder Schematic

Simulation Output:

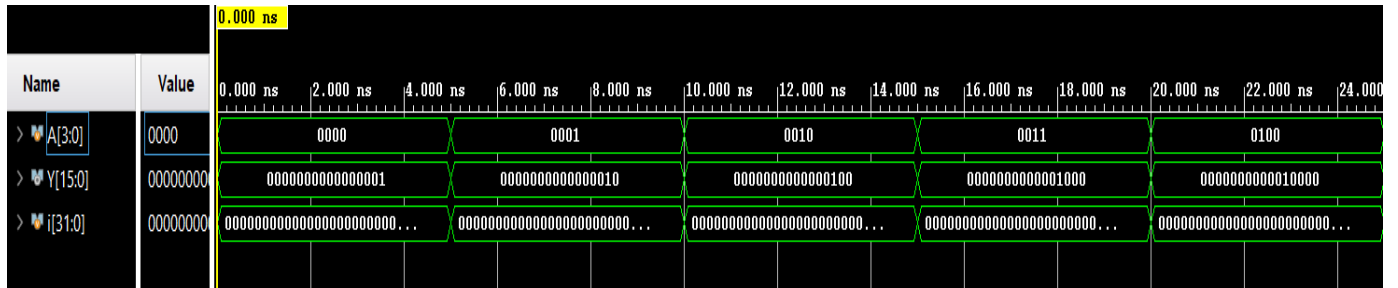

GitHub Repository URL: <https://github.com/tusharshenoy/RTL-Day-14-Decoder>