

30 Days of RTL Coding

-By T Tushar Shenoy

Day 27

Problem Statement: Implementing a 16x4 ROM.

Theory:

ROM

Read-only memory (ROM) is a data storage device used in personal computers (PCs) and other electronic devices to store information securely. It houses programs or software instructions and includes the programming required to start a computer, which is required for boot-up. It also conducts significant input/output duties. The alteration of this sort of memory, known as "firmware," has been a source of design concern throughout the growth of the contemporary computer.

Because ROM is read-only memory, it can't be modified; it's also permanent and non-volatile, which means it keeps its data even if the power is turned off. Random-access memory (RAM), on the other hand, is volatile; when power is turned off, it is gone. The phrase "non-volatile memory," which is comparable, can be applied here. In its long-term state, ROM in computer is "stateful," whereas RAM is "stateless."

ROM in Computer has the Following Characteristics:

- Non-volatile memory is referred to as ROM.
- The information saved in ROM is irreversible.
- We can only read the information and applications stored on it.
- In binary format, information and applications are stored on ROM.
- It's utilized throughout the computer's boot-up procedure.

Types of ROM

They are four types of ROM in the computer:

- MROM (Masked read-only memory)
- PROM (Programmable read-only memory)
- EPROM (Erasable programmable read-only memory)
- EEPROM (Electrically erasable programmable read-only memory)

 


FIG: 16x4 ROM

Verilog Code:

//Verilog Code for 16x4 ROM

```
module ROM(clk,enable,address,data_out);
```

```
input clk,enable;
```

```
input [3:0]address;
```

```
output reg [3:0]data_out;
```

```
reg [3:0]mem[15:0];
```

```
always@(posedge clk)
```

```
begin
```

```
    if(enable)
```

```
        data_out<=mem[address];
```

```
    else
```

```
        data_out<=4'bxxxx;
```

```
end
```

```
initial begin
```

```
mem[0]=4'b1111;
```

```
mem[1]=4'b1110;
```

```
mem[2]=4'b1101;
```

```
mem[3]=4'b1100;
```

```
mem[4]=4'b1011;
```

```
mem[5]=4'b1010;
```

```
mem[6]=4'b1001;
```

```
mem[7]=4'b1000;
```

```
mem[8]=4'b0111;
```

```
mem[9]=4'b0110;  
mem[10]=4'b0101;  
mem[11]=4'b0100;  
mem[12]=4'b0011;  
mem[13]=4'b1010;  
mem[14]=4'b0001;  
mem[15]=4'b0000;  
end
```

```
endmodule
```

Testbench Code:

//Testbench Code for 16x4 ROM

```
module ROM_tb();
```

```
    reg clk,enable;
```

```
    reg [3:0]address;
```

```
    wire [3:0]data_out;
```

```
    ROM dut(.clk(clk),.enable(enable),.address(address),.data_out(data_out));
```

```
    initial begin
```

```
        clk=1'b0;
```

```
        enable=1'b0;
```

```
        #10;
```

```
        enable=1'b1;
```

```
        address=4'b1010;
```

```
        #10;
```

```
        address=4'b1001;
```

```
        #10;
```

```
        address=4'b1000;
```

```
        #10;
```

```
        address=4'b0010;
```

```
        #10;
```

```
        address=4'b0001;
```

```
        #10;
```

```
        address=4'b1111;
```

```
        #10;
```

```
address=4'b1110;
```

```
#10;
```

```
address=4'b1101;
```

```
#10;
```

```
address=4'b1100;
```

```
#10 $finish;
```

```
end
```

```
always #4 clk=~clk;
```

```
endmodule
```

Schematic:


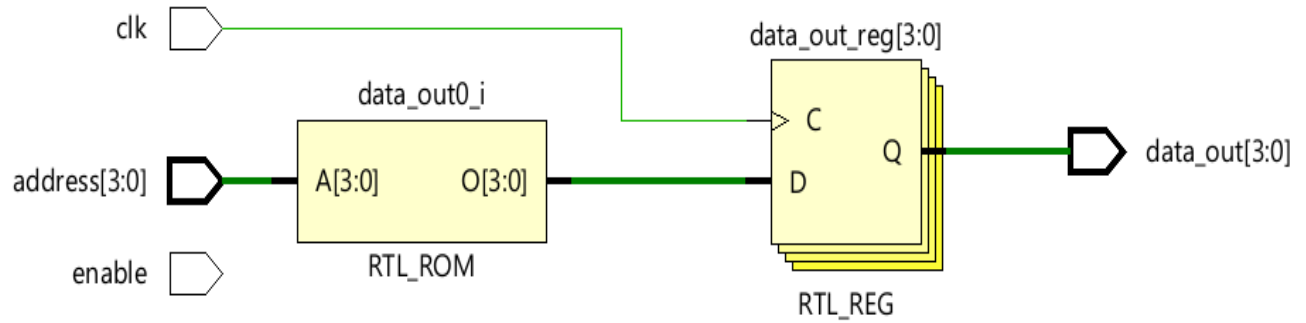


Fig: 16x4 ROM

Simulation Output:

 

GitHub Repository URL: <https://github.com/tusharshenoy/RTL-Day-27-16x4-ROM>