

# **30 Days of RTL Coding**

**-By T Tushar Shenoy**

## **Day 17**

### **Problem Statement:** Implementing Shift Registers –Part II

- 3. Parallel In Serial Out
- 4. Parallel In Parallel Out

Using Structural Style of Implementation.

### **Theory:**

#### **Parallel IN Serial OUT**


In the "Parallel IN Serial OUT" register, the data is entered in a parallel way, and the outcome comes serially. A four-bit "Parallel IN Serial OUT" register is designed below. The input of the flip flop is the output of the previous Flip Flop. The input and outputs are connected through the combinational circuit. Through this combinational circuit, the binary input  $B_0$ ,  $B_1$ ,  $B_2$ ,  $B_3$  are passed. The shift mode and the load mode are the two modes in which the "PISO" circuit works.

#### **Load mode**

The bits  $B_0$ ,  $B_1$ ,  $B_2$ , and  $B_3$  are passed to the corresponding flip flops when the second, fourth, and sixth "AND" gates are active. These gates are active when the shift or load bar line set to 0. The binary inputs  $B_0$ ,  $B_1$ ,  $B_2$ , and  $B_3$  will be loaded into the respective flip-flops when the edge of the clock is high. Thus, parallel loading occurs.

#### **Shift mode**

The second, fourth, and sixth gates are inactive when the load and shift line set to 0. So, we are not able to load data in a parallel way. At this time, the first, third, and fifth gates will be activated, and the shifting of the data will be left to the right bit. In this way, the "Parallel IN Serial OUT" operation occurs.

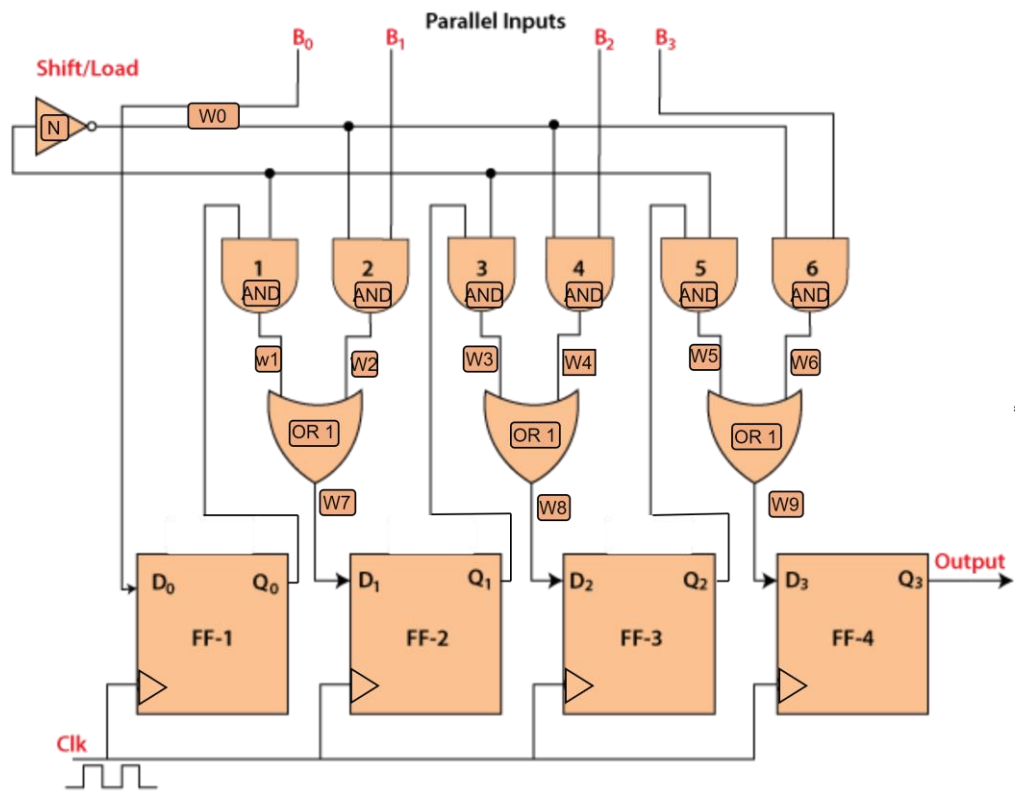

**FIG: Parallel IN Serial OUT Shift Register**

## **Verilog Code:**

//Verilog Code for D Flip Flop

```
module D_Flip_Flop(D, reset, clk, Q, Qb);
```

```
input D, reset, clk;
```

```
output reg Q, Qb;
```

```
always @(posedge clk,posedge reset)
```

```
begin
```

```
if (reset == 1)
```

```
Q<=1'b0;
```

```
else
```

```
begin
```

```
Q<=D;
```

```
end
```

```
Qb<=~Q;
```

```
end
```

```
endmodule
```

//Verilog Code for Parallel in Serial out Shift Register

```
module PISO_Shift_Register(B,SL,clk,reset,Q);
```

```
input [3:0]B;
```

```
input SL,clk,reset;
```

```
output[3:0]Q;
```

```
wire [9:0]w;
```

```
not N(w[0],SL);
```

```
and A1(w[1],SL,Q[0]);  
and A2(w[2],w[0],B[1]);  
and A3(w[3],SL,Q[1]);  
and A4(w[4],w[0],B[2]);  
and A5(w[5],SL,Q[2]);  
and A6(w[6],w[0],B[3]);
```

```
or O1(w[7],w[1],w[2]);  
or O2(w[8],w[3],w[4]);  
or O3(w[9],w[5],w[6]);
```

```
D_Flip_Flop FF1(.D(B[0]),.reset(reset),.clk(clk),.Q(Q[0]));
```

```
D_Flip_Flop FF2(.D(w[7]),.reset(reset),.clk(clk),.Q(Q[1]));
```

```
D_Flip_Flop FF3(.D(w[8]),.reset(reset),.clk(clk),.Q(Q[2]));
```

```
D_Flip_Flop FF4(.D(w[9]),.reset(reset),.clk(clk),.Q(Q[3]));
```

```
endmodule
```

## **Testbench Code:**

//Testbench Code for Serial in Parallel in Serial out Shift Register

```
module PISO_Shift_Register_tb();
```

```
    reg [3:0]B;
```

```
    reg SL,clk,reset;
```

```
    wire [3:0]Q;
```

```
    PISO_Shift_Register dut(.B(B),.SL(SL),.clk(clk),.reset(reset),.Q(Q));
```

```
    initial begin
```

```
        SL=1'b0;
```

```
        B=4'b1010;
```

```
        clk=1'b0;
```

```
        reset=1'b1;
```

```
        #6 reset=1'b0;
```

```
        #40 SL=1'b1;
```

```
        //Add More test Cases Here
```


```
        #50 $finish;
```

```
    end
```

```
    always #5 clk=~clk;
```


```
endmodule
```

# Simulation Output:

 

## Parallel IN Parallel OUT

In "Parallel IN Parallel OUT", the inputs and the outputs come in a parallel way in the register. The inputs  $B_0$ ,  $B_1$ ,  $B_2$ , and  $B_3$ , are directly passed to the data inputs  $D_0$ ,  $D_1$ ,  $D_2$ , and  $D_3$  of the respective flip flop. The bits of the binary input is loaded to the flip flops when the Positive clock edge is applied. The clock pulse is required for loading all the bits. At the output side, the loaded bits appear.

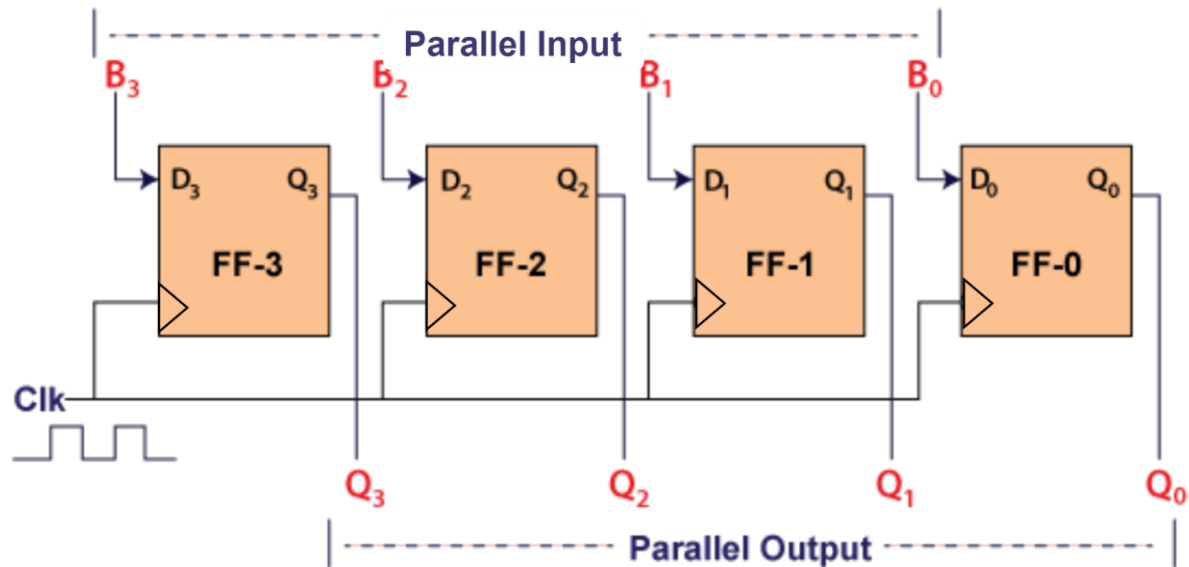

**FIG: Parallel IN Parallel OUT Shift Register**

## Verilog Code:

//Verilog Code for D Flip Flop

```
module D_Flip_Flop(D, reset, clk, Q, Qb);
```

```
input D, reset, clk;
```

```
output reg Q, Qb;
```

```
always @(posedge clk,posedge reset)
```

```
begin
```

```
if (reset == 1)
```

```
Q<=1'b0;
```

```
else
```

```
begin
```

```
Q<=D;
```

```
end
```

```
Qb<=~Q;
```

```
end
```

```
endmodule
```



//Verilog Code for Parallel in Parallel out Shift Register

module PIPO\_Shift\_Register(B,clk,reset,Q);

input [3:0]B;

input clk,reset;

output[3:0]Q;

D\_Flip\_Flop FF3(.D(B[3]),.reset(reset),.clk(clk),.Q(Q[3]));

D\_Flip\_Flop FF2(.D(B[2]),.reset(reset),.clk(clk),.Q(Q[2]));

D\_Flip\_Flop FF1(.D(B[1]),.reset(reset),.clk(clk),.Q(Q[1]));

D\_Flip\_Flop FF0(.D(B[0]),.reset(reset),.clk(clk),.Q(Q[0]));

endmodule

## **Testbench Code:**

//Testbench Code for Parallel in Parallel out Shift Register

```
module PIPO_Shift_Register_tb();
```

```
    reg [3:0]B;
```

```
    reg clk,reset;
```

```
    wire [3:0]Q;
```

```
    PIPO_Shift_Register dut(.B(B),.clk(clk),.reset(reset),.Q(Q));
```

```
    initial begin
```

```
        B=4'b0000;
```

```
        clk=1'b0;
```

```
        reset=1'b1;
```

```
        #6 reset=1'b0;
```

```
        #8 B=4'b1010;
```

```
        #8 B=4'b0011;
```

```
        #8 B=4'b1001;
```

```
        #8 B=4'b0110;
```

```
        #18 B=4'b0101;
```

```
        //Add More test Cases Here
```


```
        #8 $finish;
```

```
    end
```

```
    always #5 clk=~clk;
```

```
endmodule
```

## Simulation Output:

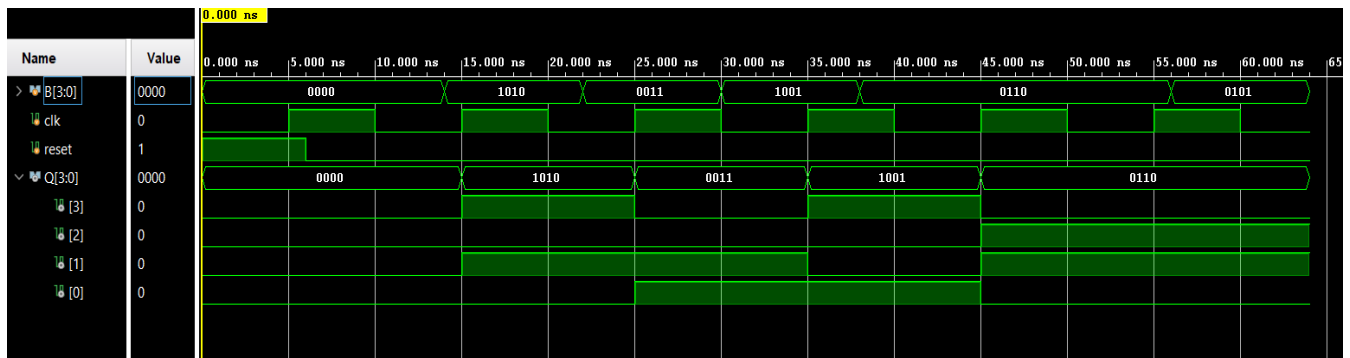

GitHub Repository URL: <https://github.com/tusharshenoy/RTL-Day-17-Shift-Registers-II>