

30 Days of RTL Coding

-By T Tushar Shenoy

Day 20

Problem Statement: Implementing 101 Sequence Detector Mealy machine.

Theory:

A sequence detector is a sequential state machine that takes an input string of bits and generates an output 1 whenever the target sequence has been detected. In a Mealy machine, output depends on the present state and the external input (x). Hence, in the diagram, the output is written outside the states, along with inputs. Sequence detector is of two types:

1. Overlapping
2. Non-Overlapping

In an overlapping sequence detector, the last bit of one sequence becomes the first bit of the next sequence. However, in a non-overlapping sequence detector, the last bit of one sequence does not become the first bit of the next sequence.

Examples:

For non overlapping case

Input :0110101011001

Output:0000100010000

For overlapping case

Input :0110101011001

Output:0000101010000

Mealey Machine 101 Sequence Detector non Overlapping

 


FIG: State Diagram of Mealey Machine 101 Sequence Detector non Overlapping

Verilog Code:

//Verilog Code for 101 Sequence Detector (Mealey Machine non Overlapping)

```
module fsm_detector_mealey(
```

```
    input in,
```

```
    input clk,
```

```
    input reset,
```

```
    output reg out
```

```
);
```

```
// Registers to hold the current and next states
```

```
reg [1:0]currentstate;
```

```
reg [1:0]nextstate;
```

```
//parameters representing different states
```

```
parameter s0=2'b00;
```

```
parameter s1=2'b01;
```

```
parameter s2=2'b10;
```

```
always@(posedge clk)
```

```
begin
```

```
if(reset)
```

```
begin
```

```
out=1'b0;
```

```
currentstate=1'b0;
```

```
nextstate=1'b0;
```

```
end
```

```
else
```

```
begin
```

```
currentstate=nextstate;
```

```
case(currentstate)
```

```
s0: if(in) // Check if input is true
```

```
begin
```

```
out=1'b0; // Set output to 0
```

```
nextstate=s1; // Transition to state s1
```

```
end
```

```
else
```

```
begin
```

```
out=1'b0; // Set output to 0
```

```
nextstate=s0; // Stay in state s0
```

```
end
```

```
s1: if(in) // Check if input is true
    begin
        out=1'b0; // Set output to 0
        nextstate=s1; // Stay in state s1
    end
    else
    begin
        out=1'b0; // Set output to 0
        nextstate=s2; // Transition to state s2
    end
s2: if(in) // Check if input is true
    begin
        out=1'b1; // Set output to 1
        nextstate=s0; // Transition to state s0
    end
    else
    begin
        out=1'b0; // Set output to 0
        nextstate=s0; // Transition to state s0
    end
endcase
end
end
endmodule
```

Testbench Code:

//Testbench Code for 101 Sequence Detector (Mealey Machine non Overlapping)

```
module fsm_detector_mealey_tb();
```

```
reg in;
```

```
reg clk;
```

```
reg reset;
```

```
wire out;
```

```
fsm_detector_mealey dut(.in(in),.clk(clk),.reset(reset),.out(out));
```

```
initial begin
```

```
    in=1'b0; // Initialize input
```

```
    clk=1'b0; // Initialize clock
```

```
    reset=1'b0; // Initialize reset
```

```
    #10;
```

```
    reset=1'b1; // Assert reset
```

```
    #10;
```

```
    reset=1'b0; // Deassert reset
```

```
    // Giving the inputs
```

```
    # 10 in=1'b0;
```

```
    # 10 in=1'b1;
```

```
    # 10 in=1'b0;
```

10 in=1'b1;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b1;
10 in=1'b1;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b0;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b1;
10 in=1'b1;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;

```
# 10 in=1'b0;
```

```
# 10 in=1'b1;
```

```
# 10 in=1'b0;
```


```
$finish;
```

```
end
```


```
always #5 clk=~clk; // Toggle clock
```

```
endmodule
```

Schematic:

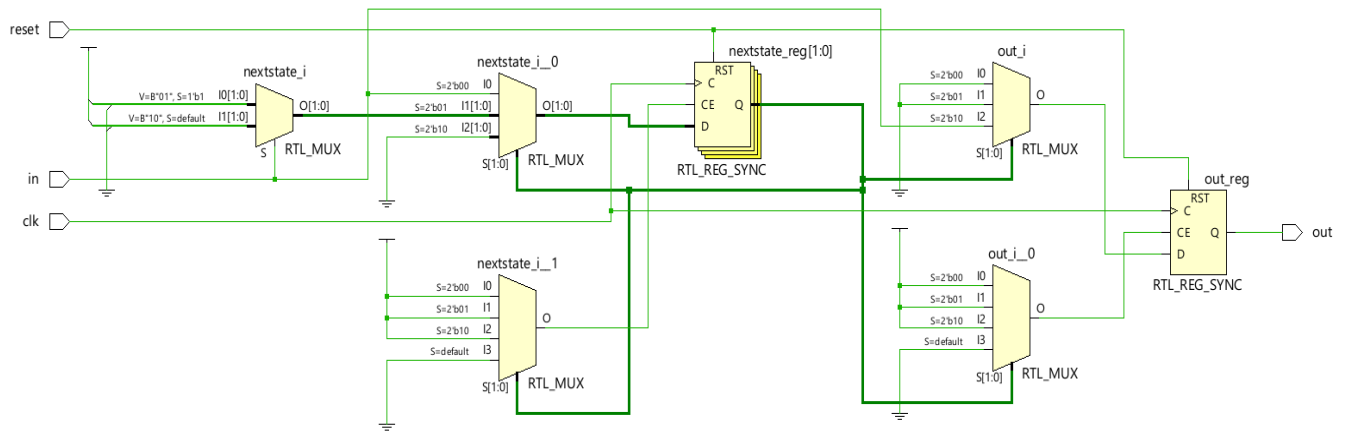

Simulation Output:

 

Mealey Machine 101 Sequence Detector Overlapping

 


FIG: State Diagram of Mealey Machine 101 Sequence Detector Overlapping

Verilog Code:

//Verilog Code for 101 Sequence Detector (Mealey Machine Overlapping)

```
module fsm_detector_mealeyo(
```

```
    input in,
```

```
    input clk,
```

```
    input reset,
```

```
    output reg out
```

```
);
```

```
// Registers to hold the current and next states
```

```
reg [1:0]currentstate;
```

```
reg [1:0]nextstate;
```

```
//parameters representing different states
```

```
parameter s0=2'b00;
```

```
parameter s1=2'b01;
```

```
parameter s2=2'b10;
```

```
always@(posedge clk)
```

```
begin
```

```
if(reset)
```

```
begin
```

```
out=1'b0;
```

```
currentstate=1'b0;
```

```
nextstate=1'b0;
```

```
end
```

```
else
```

```
begin
```

```
currentstate=nextstate;
```

```
case(currentstate)
```

```
s0: if(in) // Check if input is true
```

```
begin
```

```
out=1'b0; // Set output to 0
```

```
nextstate=s1; // Transition to state s1
```

```
end
```

```
else
```

```
begin
```

```
out=1'b0; // Set output to 0
```

```
nextstate=s0; // Stay in state s0
```

```
end
```

```
s1: if(in) // Check if input is true
    begin
        out=1'b0; // Set output to 0
        nextstate=s1; // Stay in state s1
    end
else
    begin
        out=1'b0; // Set output to 0
        nextstate=s2; // Transition to state s2
    end
s2: if(in) // Check if input is true
    begin
        out=1'b1; // Set output to 1
        nextstate=s1; // Transition to state s1
    end
else
    begin
        out=1'b0; // Set output to 0
        nextstate=s0; // Transition to state s0
    end
endcase
end
end
endmodule
```

Testbench Code:

//Testbench Code for 101 Sequence Detector (Mealey Machine Overlapping)

```
module fsm_detector_mealey_tb();
```

```
reg in;
```

```
reg clk;
```

```
reg reset;
```

```
wire out;
```

```
fsm_detector_mealeyo dut(.in(in),.clk(clk),.reset(reset),.out(out));
```

```
initial begin
```

```
    in=1'b0; // Initialize input
```

```
    clk=1'b0; // Initialize clock
```

```
    reset=1'b0; // Initialize reset
```

```
    #10;
```

```
    reset=1'b1; // Assert reset
```

```
    #10;
```

```
    reset=1'b0; // Deassert reset
```

```
    // Giving the inputs
```

```
    # 10 in=1'b0;
```

```
    # 10 in=1'b1;
```

```
    # 10 in=1'b0;
```

```
    # 10 in=1'b1;
```

10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b1;
10 in=1'b1;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b0;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b1;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b1;
10 in=1'b0;
10 in=1'b0;
10 in=1'b0;

```
# 10 in=1'b1;
```

```
# 10 in=1'b0;
```


```
$finish;
```

```
end
```


```
always #5 clk=~clk; // Toggle clock
```

```
endmodule
```

Schematic:

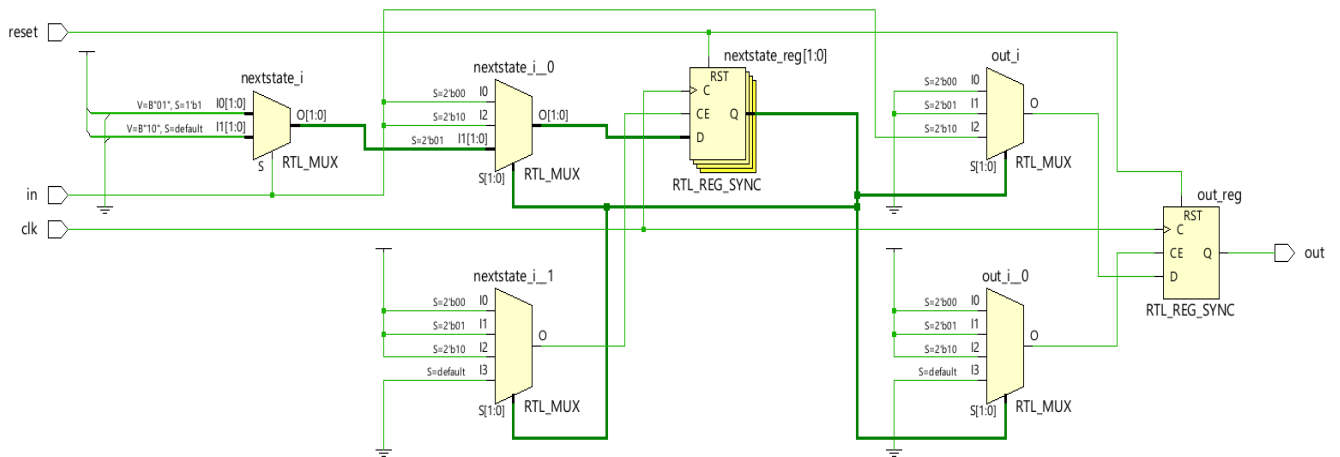

Simulation Output:

 

GitHub Repository URL: <https://github.com/tusharshenoy/RTL-Day-20-Mealey-Machine>