

30 Days of RTL Coding

-By T Tushar Shenoy

Day 29

Problem Statement: Implementing Carry Look Ahead Adder.

Theory:

A **carry-look ahead adder** (CLA) or **fast adder** is a type of electronics adder used in digital logic. A carry-look ahead adder improves speed by reducing the amount of time required to determine carry bits. It can be contrasted with the simpler, but usually slower, ripple-carry adder (RCA), for which the carry bit is calculated alongside the sum bit, and each stage must wait until the previous carry bit has been calculated to begin calculating its own sum bit and carry bit. The carry-look ahead adder calculates one or more carry bits before the sum, which reduces the wait time to calculate the result of the larger-value bits of the adder.

Advantages of Carry Look-ahead Adder

In this adder, the propagation delay is reduced. The carry output at any stage is dependent only on the initial carry bit of the beginning stage. Using this adder it is possible to calculate the intermediate results. This adder is the fastest adder used for computation.

Applications


High-speed Carry Look-ahead Adders are used as implemented as IC's. Hence, it is easy to embed the adder in circuits. By combining two or more adders calculations of higher bit Boolean functions can be done easily. Here the increase in the number of gates is also moderate when used for higher bits.

For this Adder there is a trade-off between area and speed. When used for higher bit calculations, it provides high speed but the complexity of the circuit is also increased thereby increasing the area occupied by the circuit. This adder is usually implemented as 4-bit modules which are cascaded together when used for higher calculations. This adder is costlier compared to other adders.

For Boolean computation in computers, adders are being used regularly. Charles Babbage implemented a mechanism for anticipating the carry bit in computers, to reduce the delay caused by the ripple carry adders. While designing a system, the speed of computation is the highest deciding factor for

a designer. In 1957, Gerald B. Rosenberger patented the modern Binary Carry Look-ahead Adder. Based on the analysis of gate delay and simulation, experiments are being conducted to modify the circuit of this adder to make it even faster.

Carry Look Ahead logic

 

In this circuit, the 2 internal signals P_i and G_i are given by:

$$P_i = A_i \oplus B_i \dots\dots\dots(1)$$

$$G_i = A_i B_i \dots\dots\dots(2)$$

The output sum and carry can be defined as :

$$S_i = P_i \oplus C_i \dots\dots\dots(3)$$

$$C_{i+1} = G_i + P_i C_i \dots\dots\dots(4)$$

G_i is known as the **carry Generate** signal since a carry (C_{i+1}) is generated whenever $G_i = 1$, regardless of the input carry (C_i).

P_i is known as the **carry propagate** signal since whenever $P_i = 1$, the input carry is propagated to the output carry, i.e., $C_{i+1} = C_i$ (note that whenever $P_i = 1$, $G_i = 0$).

$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

 


FIG: Carry Look ahead Block

Verilog Code:

//Verilog Code for 1 Bit Full-adder

```
module full_adder_1bit(a,b,cin,sum);
```

```
input a,b,cin;
```

```
output sum;
```

```
assign sum=a^b^cin;
```

```
endmodule
```

//Verilog Code for Carry Look Ahead Adder

```
module carry_look_ahead_adder(A,B,Cin,S,Cout);
```

```
input [3:0]A,B;
```

```
input Cin;
```

```
output [3:0]S;
```

```
output Cout;
```

```
wire C1,C2,C3;
```

```
full_adder_1bit F0(A[0],B[0],Cin,S[0]);
```

```
full_adder_1bit F1(A[1],B[1],C1,S[1]);
```

```
full_adder_1bit F2(A[2],B[2],C2,S[2]);
```

```
full_adder_1bit F3(A[3],B[3],C3,S[3]);
```

```
wire [3:0]P,G;
```

```
assign P[0]=A[0]^B[0];
```

assign P[1]=A[1]^B[1];

assign P[2]=A[2]^B[2];

assign P[3]=A[3]^B[3];

assign G[0]=A[0]&B[0];

assign G[1]=A[1]&B[1];

assign G[2]=A[2]&B[2];

assign G[3]=A[3]&B[3];

assign C1=G[0]|(P[0]&Cin);

assign C2=G[1]|(P[1]&G[0])|(P[1]&P[0]&Cin);

assign C3=G[2]|(P[2]&G[1])|(P[2]&P[1]&G[0])|(P[2]&P[1]&P[0]&Cin);

assign

Cout=G[3]|(P[3]&G[2])|(P[3]&P[2]&G[1])|(P[3]&P[2]&P[1]&G[0])|(P[3]&P[2]&P[1]&P[0]&Cin);

endmodule

Testbench Code:

//Verilog Testbench Code for Carry Look Ahead Adder

```
module carry_look_ahead_adder_tb();
```

```
    reg [3:0]A,B;
```

```
    reg Cin;
```

```
    wire [3:0]S;
```

```
    wire Cout;
```

```
    carry_look_ahead_adder dut(.A(A),.B(B),.Cin(Cin),.S(S),.Cout(Cout));
```

```
    initial begin
```

```
        A=4'b0000;B=4'b0000;Cin=0;
```

```
        #5 A=4'b0001;B=4'b0001;
```

```
        #5 A=4'b0010;B=4'b0010;
```

```
        #5 A=4'b0011;B=4'b0011;
```

```
        #5 A=4'b0100;B=4'b0100;
```

```
        #5 A=4'b0101;B=4'b0101;
```

```
        #5 A=4'b0110;B=4'b0110;
```

```
        #5 A=4'b0111;B=4'b0111;
```

```
        #5 A=4'b1000;B=4'b1000;
```

```
        #5 A=4'b1001;B=4'b1001;
```

```
        #5 A=4'b1010;B=4'b1010;
```

```
        #5 A=4'b1011;B=4'b1011;
```

```
        #5 A=4'b1100;B=4'b1100;
```

```
        #5 A=4'b1101;B=4'b1101;
```

```
        #5 A=4'b1110;B=4'b1110;
```

```
        #5 A=4'b1111;B=4'b1111;
```

```
    // Can Add More Cases
```

#5 \$finish;

end

endmodule

Schematic:

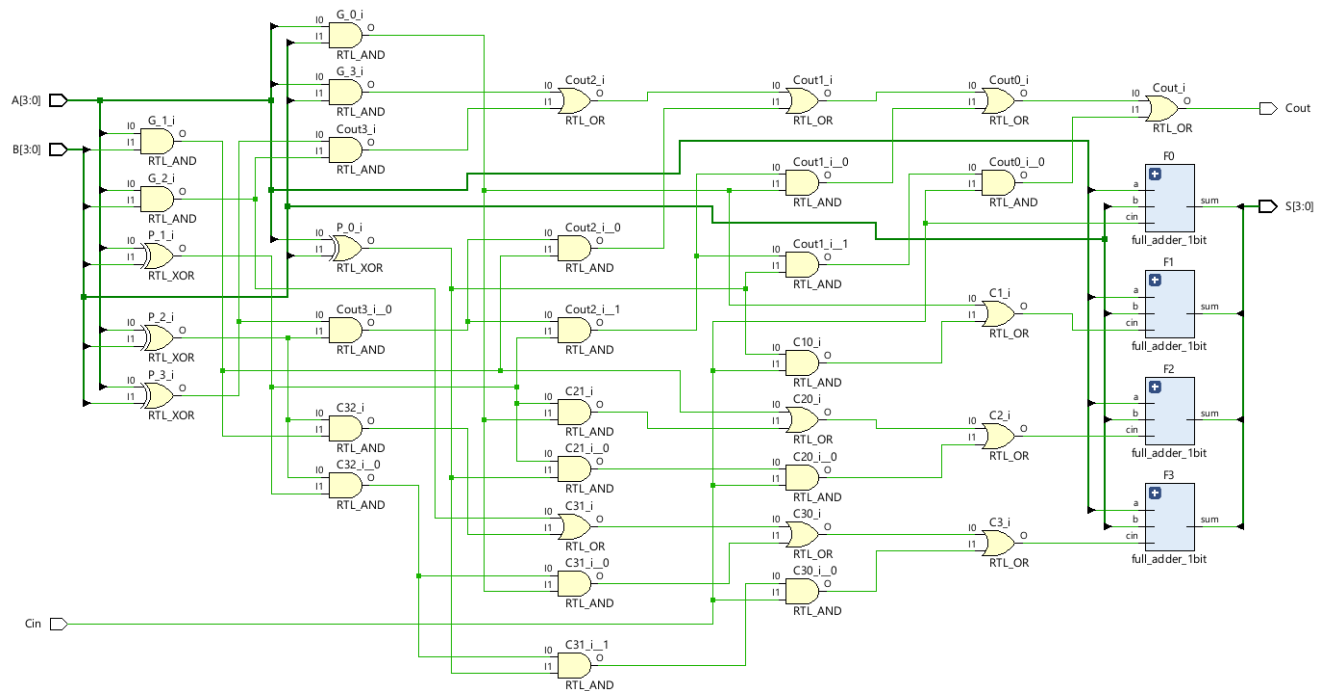


FIG Carry Look Ahead Adder

Simulation Output:

		0.000 ns																																			
		0.000 ns				10.000 ns				20.000 ns				30.000 ns				40.000 ns				50.000 ns				60.000 ns				70.000 ns				80.000 ns			
Name	Value																																				
> A[3:0]	0000	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111																				
> B[3:0]	0000	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111																				
Cin	0																																				
> S[3:0]	0000	0000	0010	0100	0110	1000	1010	1100	1110	0000	0010	0100	0110	1000	1010	1100	1110																				
Cout	0																																				

GitHub Repository URL: <https://github.com/tusharshenoy/RTL-Day-29-Carry-Look-Ahead-Adder>