

30 Days of RTL Coding

-By T Tushar Shenoy

Day 19

Problem Statement: Implementing Comparator in Gate level of Implementation.

Theory:

1-Bit Magnitude Comparator

Truth Table

Inputs		Outputs		
B	A	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

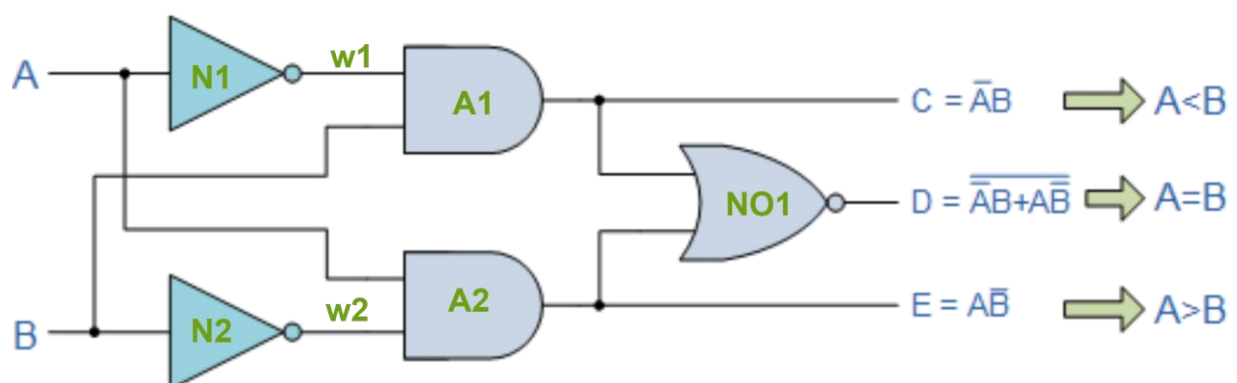


FIG: 1-Bit Magnitude Comparator

Verilog Code:

//Verilog Code for 1 Bit Comparator

```
module comparator1bit(A,B,AeB,AgB,AlB);
```

```
    input A,B;
```

```
    output AeB,AgB,AlB;
```

```
    wire w1,w2;
```

```
    not N1(w1,A);
```

```
    not N2(w2,B);
```

```
    and A1(AlB,w1,B);
```

```
    and A2(AgB,w2,A);
```

```
    nor NO1(AeB,AlB,AgB);
```

```
endmodule
```

Testbench Code:

//Testbench code for 1 Bit Comparator

```
module comparator1bit_tb();
```

```
    reg A,B;
```

```
    wire AeB,AgB,AlB;
```

```
    comparator1bit dut(.A(A),.B(B),.AeB(AeB),.AgB(AgB),.AlB(AlB));
```

```
    initial begin
```

```
        A=1'b0;B=1'b0;
```

```
        #5 A=1'b0;B=1'b1;
```

```
        #5 A=1'b1;B=1'b0;
```


```
        #5 A=1'b1;B=1'b1;
```

```
        #5 $finish;
```


```
    end
```

```
endmodule
```

Schematic:

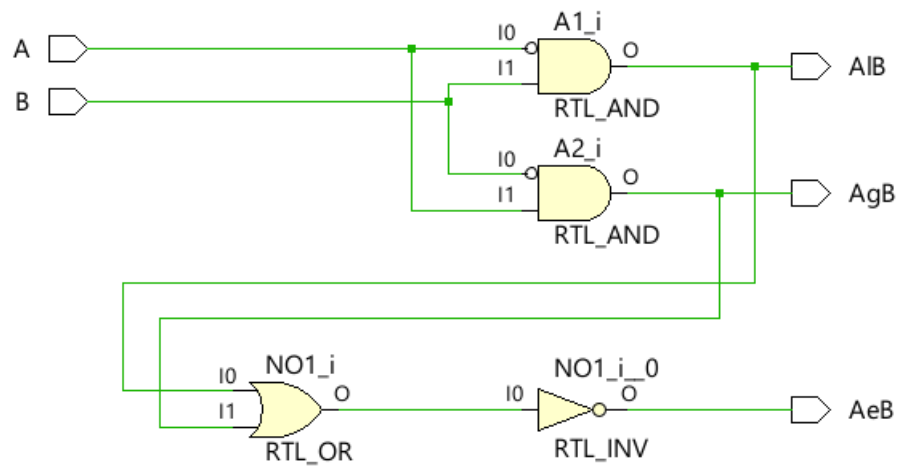

Simulation Output:

 

2-Bit Magnitude Comparator

Truth Table

Inputs				Outputs		
A		B		A = B	A > B	A < B
a1	a0	b1	b0			
0	0	0	0	1	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	1	0	0

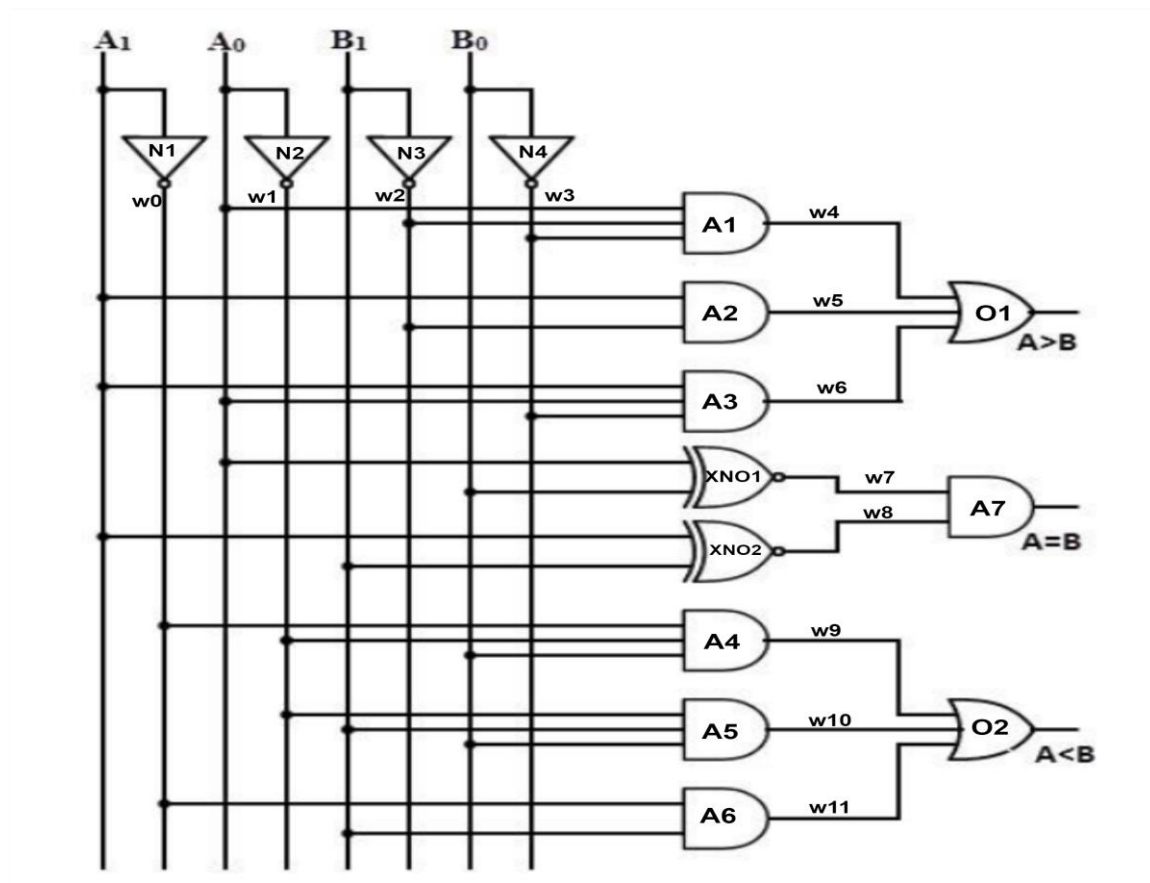


FIG: 2-Bit Magnitude Comparator

Verilog Code:

//Verilog Code for 2 Bit Comparator

```
module comparator2bit(A,B,AeB,AgB,AlB);
```

```
input [1:0]A,B;
```

```
output AeB,AgB,AlB;
```

```
wire [11:0]w;
```

```
not N1(w[0],A[1]);
```

```
not N2(w[1],A[0]);
```

```
not N3(w[2],B[1]);
```

```
not N4(w[3],B[0]);
```

```
and A1(w[4],A[0],w[2],w[3]);
```

```
and A2(w[5],A[1],w[2]);
```

```
and A3(w[6],A[1],A[0],w[3]);
```

```
or O1(AgB,w[4],w[5],w[6]);
```

```
xnor XNO1(w[7],A[0],B[0]);
```

```
xnor XNO2(w[8],A[1],B[1]);
```

```
and A7(AeB,w[7],w[8]);
```

```
and A4(w[9],w[0],w[1],B[0]);
```

```
and A5(w[10],w[1],B[1],B[0]);
```

```
and A6(w[11],w[0],B[1]);
```

```
or O2(A1B,w[9],w[10],w[11]);
```

```
endmodule
```

Testbench Code:

```
//Testbench code for 2 Bit Comparator
```

```
module comparator2bit_tb();
```

```
reg [1:0]A,B;
```

```
wire AeB,AgB,A1B;
```

```
comparator2bit dut(.A(A),.B(B),.AeB(AeB),.AgB(AgB),.A1B(A1B));
```

```
initial begin
```

```
    A=2'b00;B=2'b11;
```

```
#5 A=2'b01;B=2'b10;
```

```
#5 A=2'b10;B=2'b01;
```

```
#5 A=2'b11;B=2'b00;
```

```
#5 A=2'b00;B=2'b00;
```


```
//Add More Test Cases Here
```

```
#5 $finish;
```


```
end
```

```
endmodule
```

Schematic:

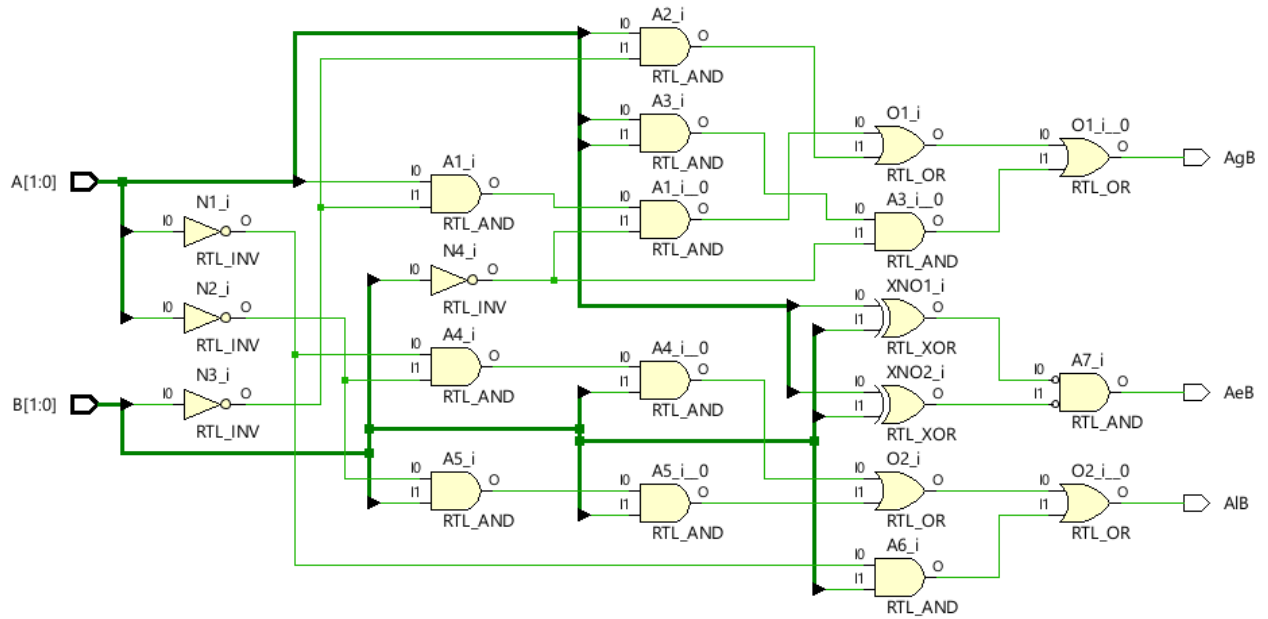

Simulation Output:

 

GitHub Repository URL: <https://github.com/tusharshenoy/RTL-Day-19-Comparator-Structural>