

30 Days of RTL Coding

-By T Tushar Shenoy

Day 24

Problem Statement: Implementing Universal Shift register in Structural Style of Modelling.

Theory:

A Universal shift register is a register which has both the right shift and left shift with parallel load capabilities. Universal shift registers are used as memory elements in computers. A Unidirectional shift register is capable of shifting in only one direction. A bidirectional shift register is capable of shifting in both the directions. The Universal shift register is a combination design of **bidirectional** shift register and a **unidirectional** shift register with parallel load provision.

S1	S0	
0	0	- Hold
0	1	- Shift Right
1	0	- Shift Left
1	1	- Parallel Load

FIG: USR Operation for different Combination of S1 and S0

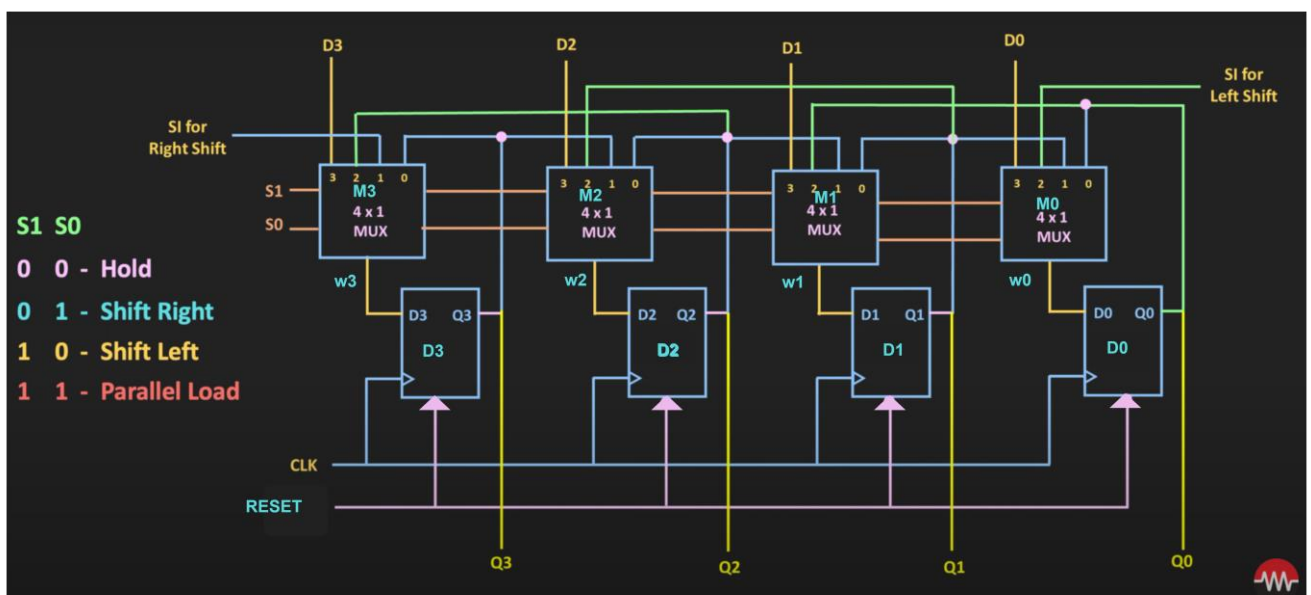


FIG: Block Diagram of USR

Verilog Code:

//Verilog Code for Mux

```
module mux_4x1(I0,I1,I2,I3,S,O);
```

```
input I0,I1,I2,I3;
```

```
input [1:0]S;
```

```
output reg O;
```

```
always@(*)
```

```
begin
```

```
case(S)
```

```
2'b00 :O<=I0;
```

```
2'b01 :O<=I1;
```

```
2'b10 :O<=I2;
```

```
2'b11 :O<=I3;
```

```
endcase
```

```
end
```

```
endmodule
```

```
// Verilog Code for D Flip Flop
module D_Flip_Flop(D, reset, clk, Q);
    input D, reset, clk;
    output reg Q;

    always @(posedge clk,posedge reset)
    begin
        if(reset)
            Q=0;
        else
            Q=D;
    end
endmodule
```

//Verilog Code for USR

module USR(D,S,clk,reset,SR,SL,Q);

input [3:0]D;

input [1:0]S;

input clk,reset,SR,SL;

output [3:0]Q;

wire [3:0]w;

mux_4x1 M3(.I0(Q[3]),.I1(SR),.I2(Q[2]),.I3(D[3]),.S(S),.O(w[3]));

mux_4x1 M2(.I0(Q[2]),.I1(Q[3]),.I2(Q[1]),.I3(D[2]),.S(S),.O(w[2]));

mux_4x1 M1(.I0(Q[1]),.I1(Q[2]),.I2(Q[0]),.I3(D[1]),.S(S),.O(w[1]));

mux_4x1 M0(.I0(Q[0]),.I1(Q[1]),.I2(SL),.I3(D[0]),.S(S),.O(w[0]));

D_Flip_Flop D3(.D(w[3]),.reset(reset),.clk(clk),.Q(Q[3]));

D_Flip_Flop D2(.D(w[2]),.reset(reset),.clk(clk),.Q(Q[2]));

D_Flip_Flop D1(.D(w[1]),.reset(reset),.clk(clk),.Q(Q[1]));

D_Flip_Flop D0(.D(w[0]),.reset(reset),.clk(clk),.Q(Q[0]));

endmodule

Testbench Code:

```
//Testbench code for USR
```

```
module USR_tb();
```

```
reg [3:0]D;
```

```
reg [1:0]S;
```

```
reg clk,reset,SR,SL;
```

```
wire [3:0]Q;
```

```
USR dut(.D(D),.S(S),.clk(clk),.reset(reset),.SR(SR),.SL(SL),.Q(Q));
```

```
initial begin
```

```
clk=1'b0;
```

```
reset=1'b1;
```

```
SR=1'b0;
```

```
SL=1'b0;
```

```
S=2'b00;    //Hold State
```

```
D=4'b0000;
```

```
#8 reset=1'b0;
```

```
#16 S=2'b01;    //Shifting Value Right
```

```
    SR=1'b1;
```

```
#8 SR=1'b1;
```

```
#8 SR=1'b1;
```

```
#8 SR=1'b1;
```

```
#16 S=2'b10;    //Shifting Value Left
```

```
    SL=1'b0;
```

```
#8 SL=1'b0;
```

```
#8 SL=1'b0;
```

```
#8 SL=1'b0;
```

```
#16 S=2'b11; //Hold
```

```
    D=4'b1010;
```

```
//ADD More Test Cases Here
```

```
#32 $finish;
```

```
end
```

```
always #5 clk=~clk;
```

```
endmodule
```

Schematic:

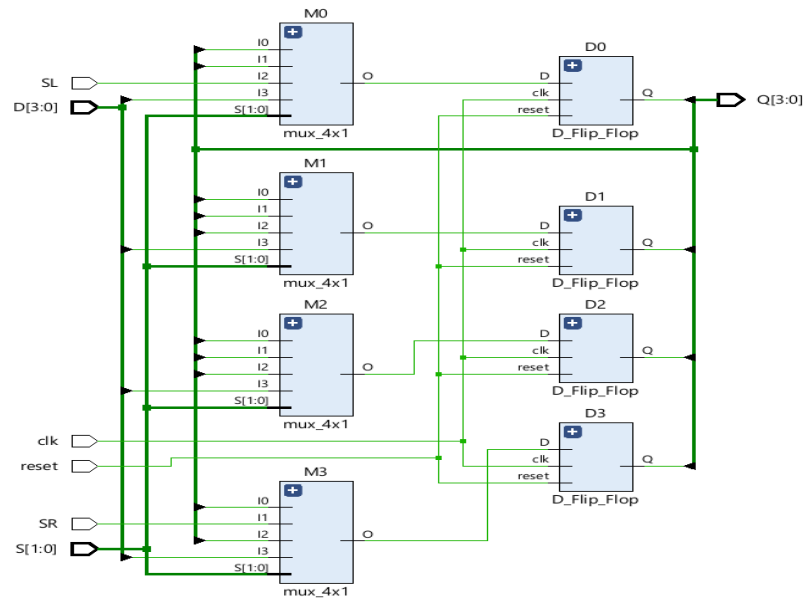


Fig: Schematic of USR

 


Fig: Schematic of 4x1 Mux


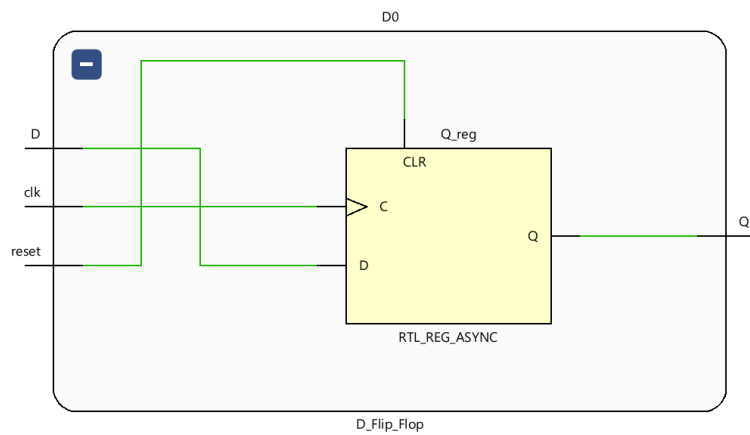


Fig: Schematic of D Flip Flop

Simulation Output:

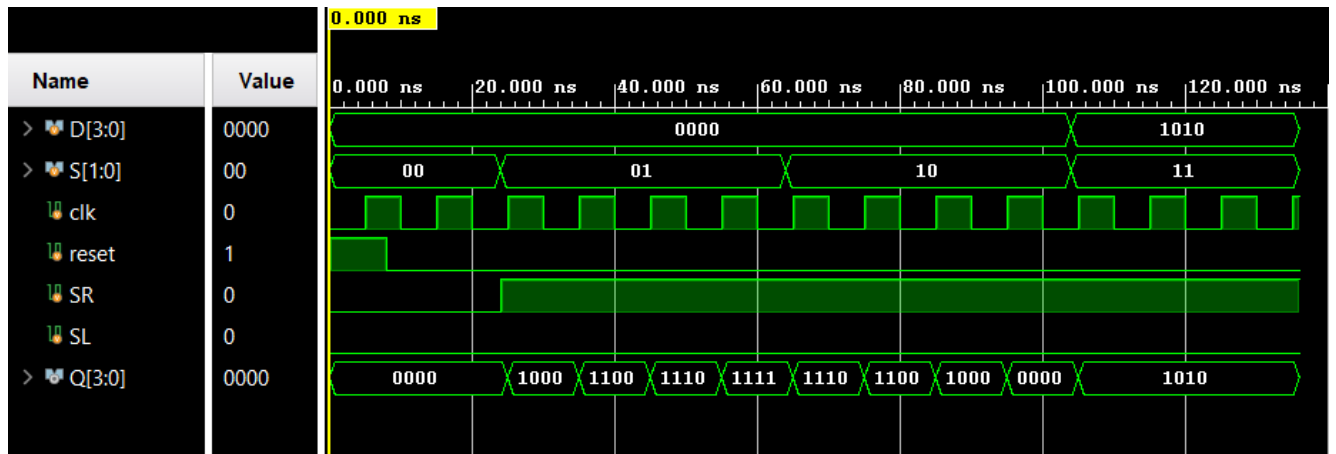

GitHub Repository URL: <https://github.com/tusharshenoy/RTL-Day-24-USR>